

Indian Institute of Information Technology, Design and
Manufacturing, Kancheepuram

System on Programmable Chip Practice


UART Communication Controller

Nehemiae G. Roy
EVD18I018

Outline


- Working Principle
- Requirement for UART
- Shift Registers
- Code
 - Transmitter Module
 - Receiver Module
 - Testbench
- Outputs
- Frequency Deviation Analysis
- Further Information
- References

Working Principle

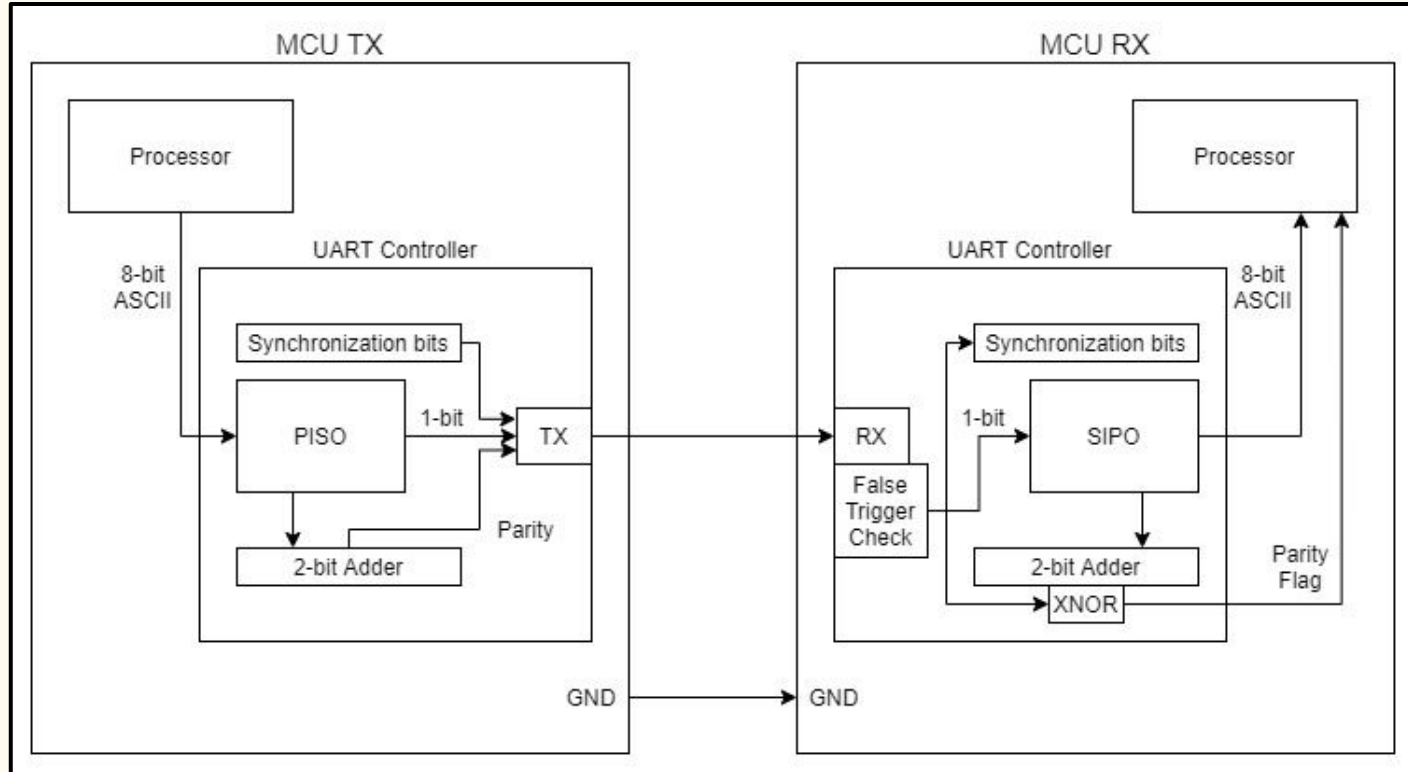

Requirements for UART


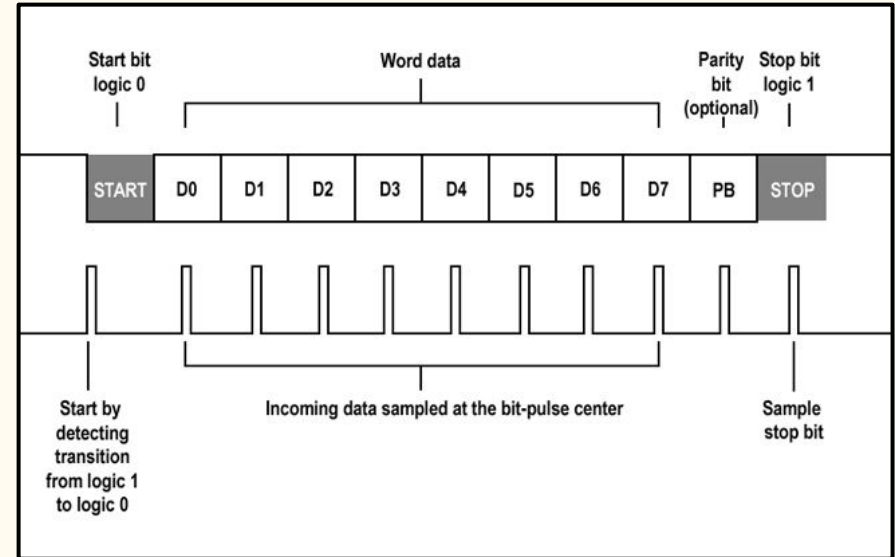
- Baud Rate
 - Baud rate generator
 - Typical speeds - 4200 bps, 9600 bps
 - Internal clock synchronization
 - Max. 10% deviation in baud rate
 - False Triggering
- Frame Structure
 - Synchronization bits
 - Idle state - HIGH
 - Data bits
 - Optional parity bit



Frame Structure

Shift Registers

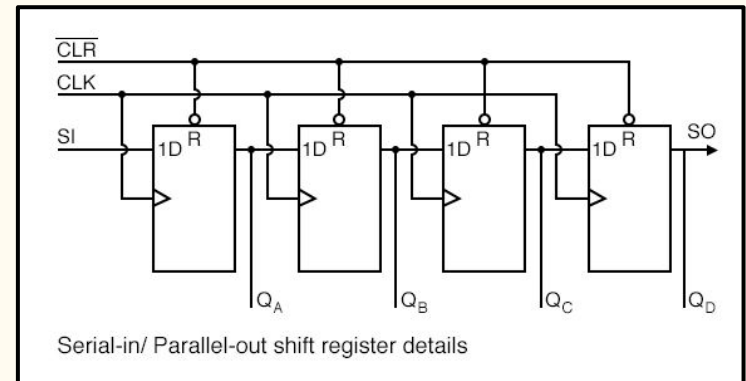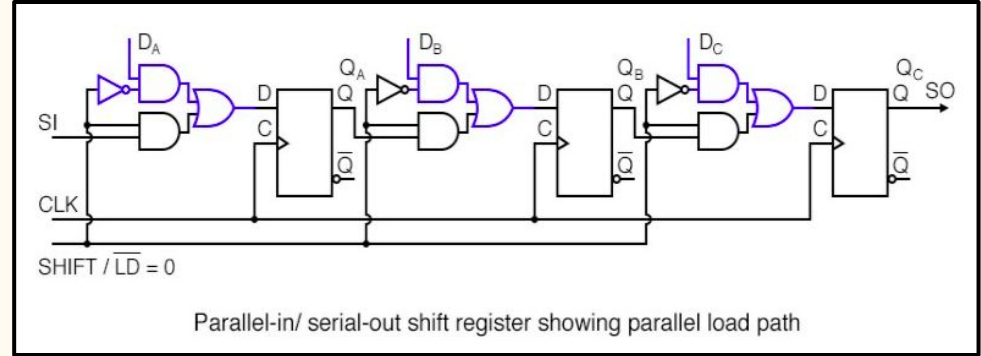- Parallel-In Serial-Out Register
 - Load/Shift
 - LSB - Start Bit
 - 4 - bit word
 - Parity Bit
 - MSB - Stop Bit
- Serial-In Parallel-Out Register
 - Read parallel data after “Stages * Time Period”



Transmitter Module

```
module Processor_TX(in_word, data_ready, CLK, tx_flag, out_bit);
input [3:0]in_word;
input data_ready, CLK;
output tx_flag, out_bit;
reg tx_flag = 0;
reg [3+3:0]data = 7'b1111111;
reg SHIFT_LD = 0;
integer time_flag = 0, clock_count = -1;

PISO_SR PSl(data, SHIFT_LD, CLK, out_bit);

always@(posedge CLK)
begin
    if (data_ready == 0)
        begin
            data = 7'b1111111;
        end
    else if ((data_ready == 1) && (time_flag == 0))
        begin
            data[0] = 0;
            data[4:1] = in_word;
            data[5] = in_word[0] ^ in_word[1] ^ in_word[2] ^ in_word[3];
            data[6] = 1;
            //data[5] = 0; //Parity Flag Trigger
            //data[6] = 0; //Break Flag Trigger
            SHIFT_LD = 0;
            time_flag = 1;
            clock_count = -1;
        end
end
```

```
        data[5] = in_word[0] ^ in_word[1] ^ in_word[2] ^ in_word[3];
        data[6] = 1;
        //data[5] = 0; //Parity Flag Trigger
        //data[6] = 0; //Break Flag Trigger
        SHIFT_LD = 0;
        time_flag = 1;
        clock_count = -1;
    end

    if (time_flag == 1)
    begin
        clock_count = clock_count + 1;
        if (clock_count == 1)
            SHIFT_LD = 1;
        else if (clock_count == 7)
            begin
                data = 7'b1111111;
                SHIFT_LD = 0;
            end
        else if (clock_count == 8)
            begin
                tx_flag = 1;
                time_flag = 0;
            end
        end
    end

end

endmodule
```

Receiver Module

```
module Processor_RX(in_bit, CLK, rx_flag, b_flag, p_flag, data);
input in_bit, CLK;
output rx_flag, b_flag, p_flag;
output [3:0]data;
reg [3:0]data;
reg rx_flag = 0, b_flag = 0, p_flag = 0;
wire [3+3:0]out_word;
integer time_flag = 0, clock_count = -1;

SIPO_SR SPI(in_bit, CLK, out_word);

always@(posedge CLK)
begin
    if ((in_bit == 0) && (time_flag == 0))
    begin
        time_flag = 1;
        clock_count = -1;
    end

    if (time_flag == 1)
    begin
        clock_count = clock_count + 1;
        if (clock_count == 7)
        begin
            rx_flag = 1;
            if (out_word[6] == 0)
                b_flag = 1;
            else if (out_word[4] ^ out_word[3] ^ out_word[2] ^ out_word[1] != out_word[5])
                p_flag = 1;
        end
    end
end
```

Receiver Module

```
SIPO_SR SPI(in_bit, CLK, out_word);

always@(posedge CLK)
begin
    if ((in_bit == 0) && (time_flag == 0))
    begin
        time_flag = 1;
        clock_count = -1;
    end

    if (time_flag == 1)
    begin
        clock_count = clock_count + 1;
        if (clock_count == 7)
        begin
            rx_flag = 1;
            if (out_word[6] == 0)
                b_flag = 1;
            else if (out_word[4] ^ out_word[3] ^ out_word[2] ^ out_word[1] != out_word[5])
                p_flag = 1;
            else
                data = out_word[4:1];
            time_flag = 0;
        end
    end
end

endmodule
```


Testbench

```
module UART_testbench();
    reg [3:0]out_word;
    reg data_ready, CLK1, CLK2;
    wire tx_flag, in_bit;
    wire rx_flag, b_flag, p_flag;
    wire [3:0]rx_word;

    Processor_TX P1(out_word, data_ready, CLK1, tx_flag, in_bit);
    Processor_RX P2(in_bit, CLK2, rx_flag, b_flag, p_flag, rx_word);


    always #50 CLK1 = ~CLK1;
    always #50 CLK2 = ~CLK2;

    initial
    begin
        out_word = 4'b1011;
        data_ready = 1;
        CLK1 <= 1;
        CLK2 <= 1;

        #(100 * 8) data_ready <= 0;
    end

endmodule
```


Idle State

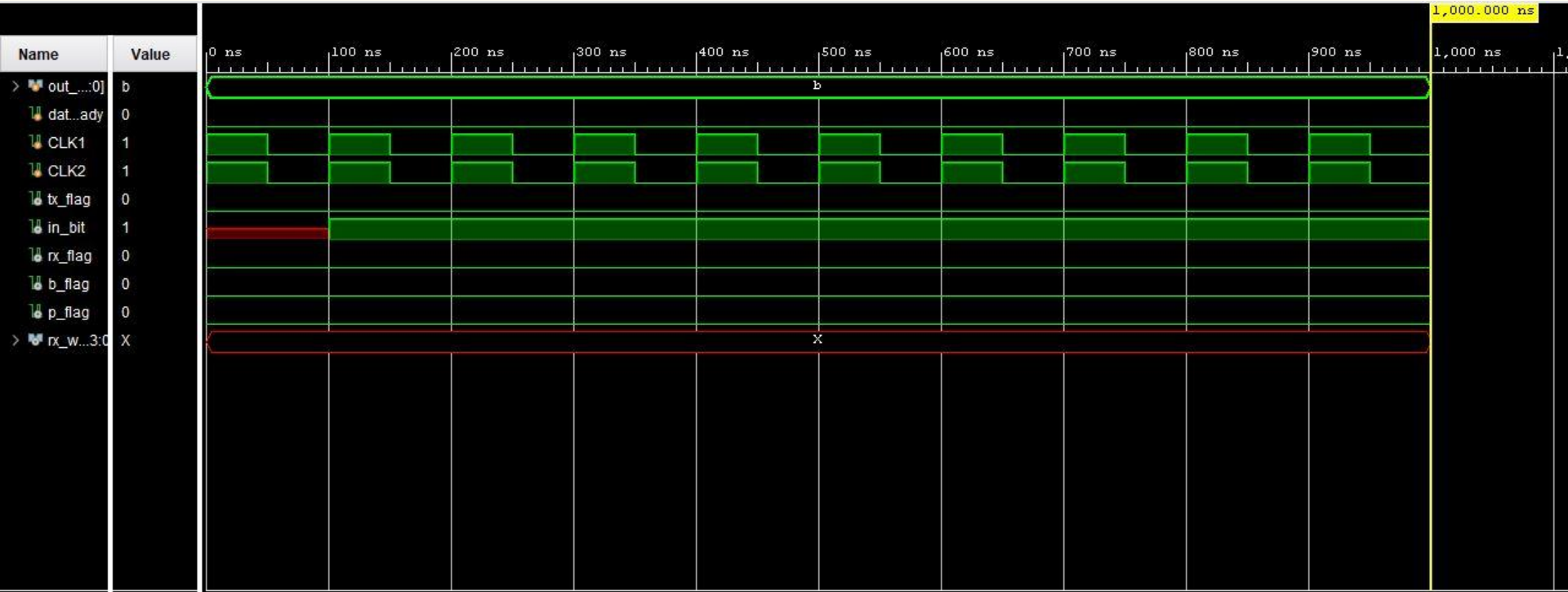


Data Transmit



Parity Flag

 

Break Flag

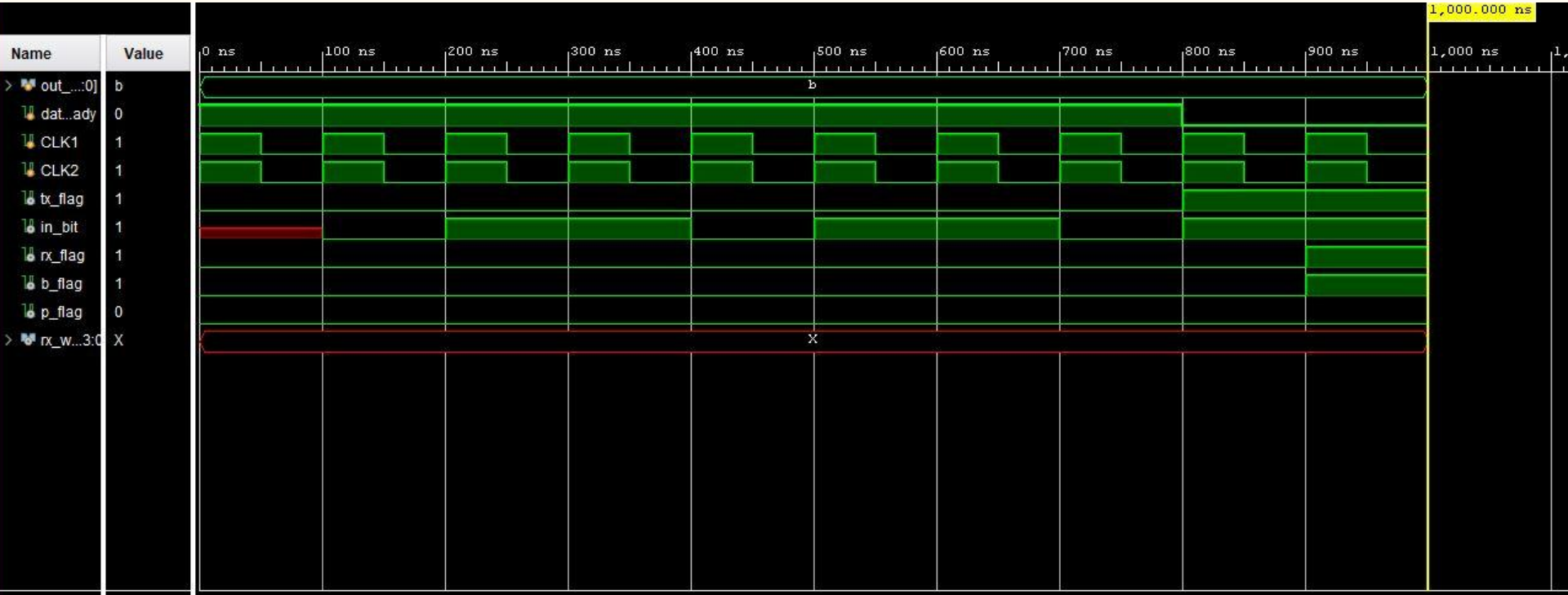


Frequency Deviation

Processor TX Time Period	Processor RX Time Period	Frequency Deviation	Status
100	100	0%	Correct
100	90	10%	Correct
100	88	12%	Correct
100	86	14%	Correct
100	84	16%	Correct
100	82	18%	Parity Error
100	80	20%	Incorrect Value

Further Information

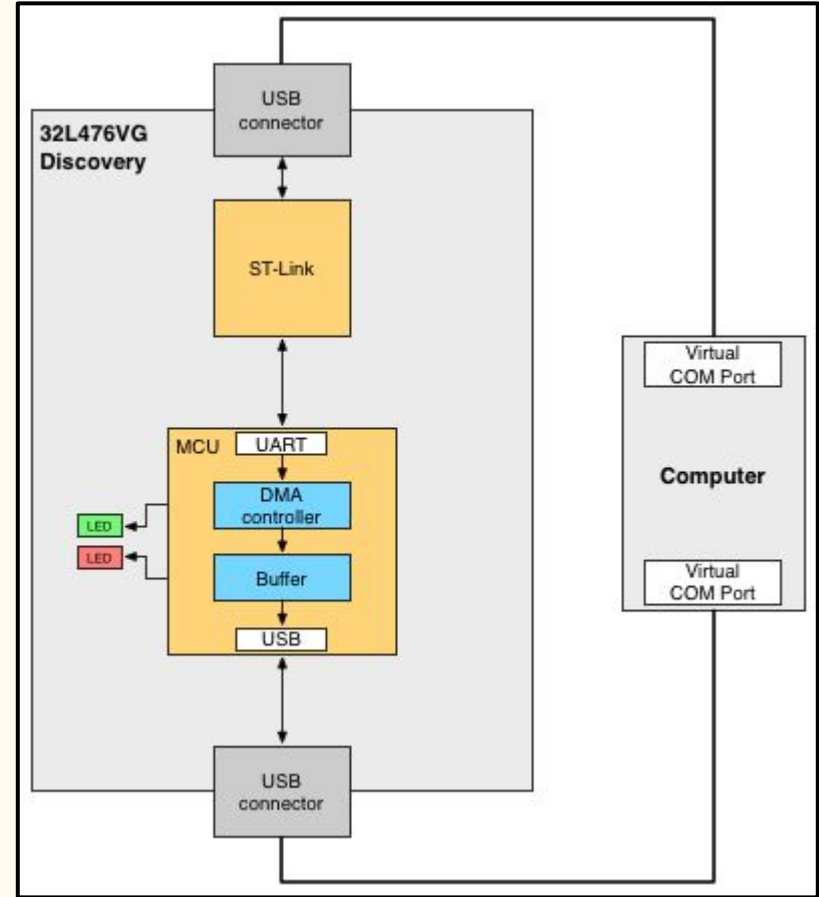- Inclusion of buffers
 - Overrun Error
- CPU Blocking
 - DMA
 - Peripheral-To-Memory
 - Double Buffering
- Applications
 - Serial Terminal
 - ASCII Characters
 - USB CDC (Virtual Com Port)



References

Websites:

1. “BASICS OF UART COMMUNICATION”, <https://www.circuitbasics.com/basics-uart-communication/>
2. “UART: A Hardware Communication Protocol Understanding Universal Asynchronous Receiver/Transmitter”,
<https://www.analog.com/en/analog-dialogue/articles/uart-a-hardware-communication-protocol.html>
3. “Universal Asynchronous Receiver-Transmitter”,
https://en.wikipedia.org/wiki/Universal_asynchronous_receiver-transmitter

Videos:

1. “Understanding UART”, https://www.youtube.com/watch?v=sTHckUyxwp8&ab_channel=RohdeSchwarz
2. “SparkFun According to Pete 9-17-12: Serial Communication Demystified”,
https://www.youtube.com/watch?v=JJZOTtwpAjA&ab_channel=SparkFunElectronics

References

Websites:

1. “The D-Type Flip-Flop”, https://www.electronics-tutorials.ws/sequential/seq_4.html
2. “Sequential Logic Circuits”, https://www.electronics-tutorials.ws/sequential/seq_1.html
3. “D Flip-Flop”,
<https://www.javatpoint.com/verilog-d-flip-flop#:~:text=D%20flip%20flop%20is%20an,the%20edge%20triggered%20always%20statements.>
4. “Shift Registers: Serial-in, Parallel-out (SIPO) Conversion”,
<https://www.allaboutcircuits.com/textbook/digital/chpt-12/serial-in-parallel-out-shift-register/>
5. “Shift Registers: Parallel-in, Serial-out (PISO) Conversion”,
<https://www.allaboutcircuits.com/textbook/digital/chpt-12/parallel-in-serial-out-shift-register/>

Research Paper:

1. “A Review Paper on Design and Simulation of UART for Serial Communication”, Vibhu Chinmay, Shubham Sachdeva, IJIRT

THANK YOU